

Lecture Topics:

- The Digital World
- Boolean Algebra
- Logic Gates & Circuits
- minterms and K-maps
- Maxterms and K-maps

THE DIGITAL WORLD

Major Application of Digital Logic: the design of processor chips in computers and mobile devices.

- **Classic iPod (4th generation 2004)**

From: electronics.howstuffworks.com/ipod3.htm



Photo credit: apple.com

- Display (320 x 240 pixel LCD)
From: electronics.howstuffworks.com/lcd2.htm
- Click Wheel (capacitive sensing controller)
From: electronics.howstuffworks.com/ipod4.htm
- PortalPlayer SOC processor (dual core)

 


Photo credit: microblog.routed.net

- Memory (SDRAM 32 MB)
- Hard drive (30 GB)
- **iPhone 16 Pro differences (2024)**
From: https://en.wikipedia.org/wiki/List_of_iOS_devices



Image credit: apple.com

- 6 GB memory
- 128-1012 GB solid-state drive
- Touch HDR display (2556 x 1179 pixel color OLED)
- 64 bit Apple A18 Pro SOC processor
 - Hex-core CPU
 - Hex-core GPU
 - 16-core NPU


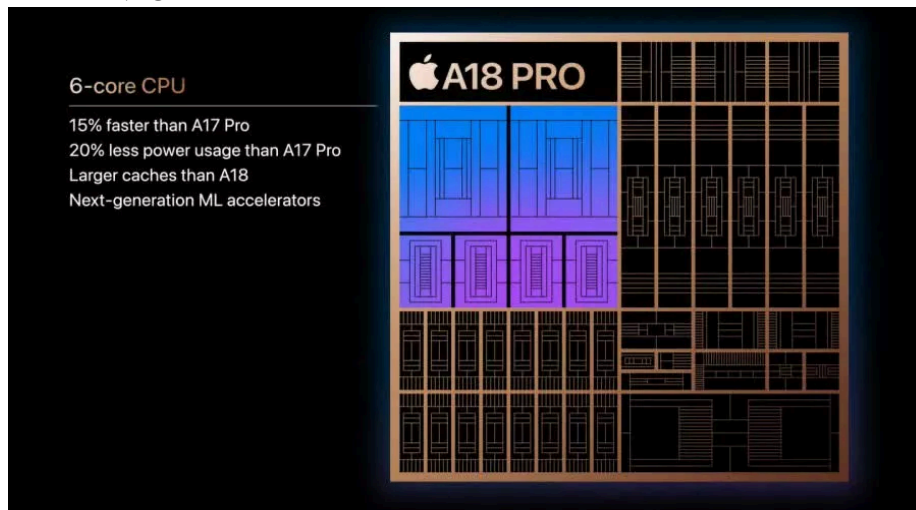


Image Credit: Apple


Digital Logic Components: these are the digital building blocks that will be studied in this course.

- **Register** (holds various forms of digital data)
- **Port** (a register interfacing data to/from the outside world)

Register:

 


Port:

 


- **ALU** (adds contents of 2 registers)

ALU:

 

- **Bus** (A path by which data may flow from one register to another in parallel)

Bus:

 

- **USB cable** (A path by which data packets may be transferred serially to ports from a hub)

USB:




- **Encoder** (Encodes or compresses data)
- **Decoder** (Decodes or expands data. Also used to make memory location selections)
- **MUX** (Selects between many data sources)


Encoder:

Decoder:


MUX:

 

 - **ROM** (An storage array that can be read word by word, chosen by an address)




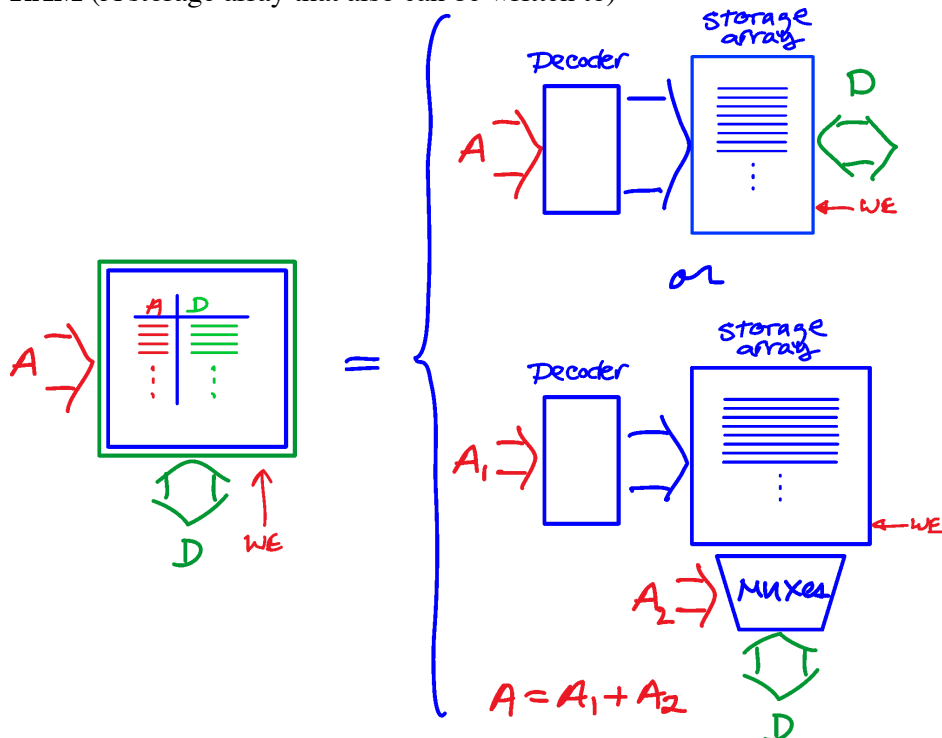- **RAM** (A storage array that also can be written to)




- **Hard Disk Drive** (A magnetic storage device from which blocks of data can be stored and read)

Hard Drive

 


- **USB drive** (A ROM device which can transfer data in blocks over a USB cable)


USB Drive (also flash or SSD)

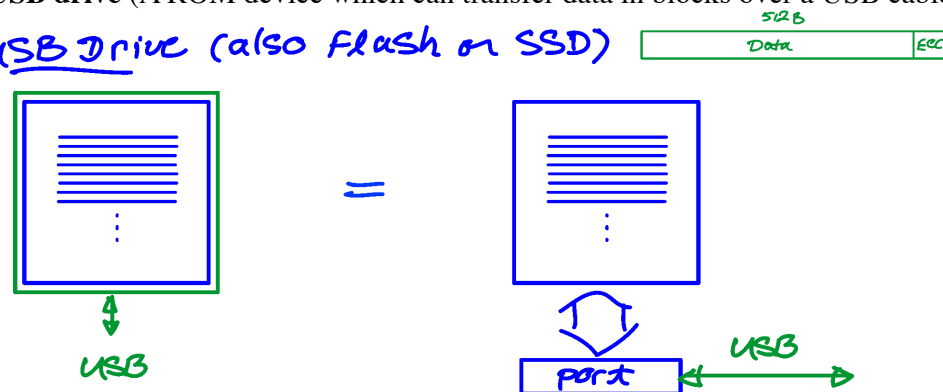

 - **Microcontroller MCU** (A processing device consisting of an ALU, registers, ports and RAM)




 - **Microprocessor CPU** (More powerful processor that has extensive memory and multiple ALUs)



- **Graphic Processing Unit GPU**

 
- The H100 consists of 144 Streaming Multiprocessors (SM)
- Each SM has a tensor core capable of fast matrix algebra



- A GPT or Grot AI Large Language Model (LLM) application requires:
 - 64-256 GPUs for inference
 - 25,000 GPUs for training

Digital Data Types

- **Numeric**

 

Graphic credit: techspirited.com

- **Beginnings:**

- bit (b) defined by Claude Shannon as "basic information digit" (1948)
 - byte (B) coined by IBM researcher Werner Buchholtz (1964)

Computer Bit



Computer Byte




ComputerHope.com

Image credit: ComputerHope.com

- A new bit used in Quantum Computing is the Qubit:

● 0

● 1

 

Classical Bit

Qubit

Image credit: IBTimes UK

o Integers in a byte (8 bits)

- Total unsigned (0 -> 255, 256 total members)

1 byte	decimal	hex	1 byte	decimal	hex	1 byte	decimal	hex
00000000	= 0	00	00001000	= 8	08	00010000	= 16	10
00000001	= 1	01	00001001	= 9	09	01100011	= 99	63
00000010	= 2	02	00001010	= 10	0A	01100100	= 100	64
00000011	= 3	03	00001011	= 11	0B	11001000	= 200	C8
00000100	= 4	04	00001100	= 12	0C	11111011	= 253	FD
00000101	= 5	05	00001101	= 13	0D	11111110	= 254	FE
00000110	= 6	06	00001110	= 14	0E	11111111	= 255	FF
00000111	= 7	07	00001111	= 15	0F			

- Example: Hexadecimal and decimal

$$\begin{array}{rcl}
 \text{7 6 5 4 3 2 1 0} \\
 \boxed{11001000} & = & 1 \times 2^7 = 128 \\
 \text{C} \quad 8 & & + 1 \times 2^6 = 64 \\
 & & + 1 \times 2^3 = 8 \\
 \hline
 \boxed{0xC8} & = & 200
 \end{array}$$

- Comparison of decimal, binary, octal and hex:

Decimal	Binary	Octal	Hexadecimal
0	0	0	0
1	1	1	1
2	10	2	2
3	11	3	3
4	100	4	4
5	101	5	5
6	110	6	6
7	111	7	7
8	1000	10	8
9	1001	11	9
10	1010	12	A
11	1011	13	B
12	1100	14	C
13	1101	15	D
14	1110	16	E
15	1111	17	F
16	10000	20	10

Red 1 and 2 = "Carry"

A,B,C,D,E,F = extra hex digits

Important number conversions to remember:

$$(10)_{10} = (1010)_2 = (A)_{16}$$

$$(11)_{10} = (1011)_2 = (B)_{16}$$

o Fractionals in a byte


- Example:

$$\begin{array}{rcl}
 \text{1 2 3 4 5 6 7 8} \\
 \boxed{11001000} & = & 1 \times 2^{-1} = .5 \\
 \text{. C} \quad 8 & & + 1 \times 2^{-2} = .25 \\
 & & + 1 \times 2^{-5} = .03125 \\
 \hline
 \boxed{0x.C8} & = & .78125
 \end{array}$$


- Integer conversions between binary, octal and hex

- Octal: group in 3 bits
- Hex: group in 4 bits

 - Example #1:
Convert $(010101100)_2$ to base 8 and 16



 - Example #2:
Convert $(110.110)_2$ to base 8 and 16



o Juxtapositional notation:

- Integer, radix point and fraction

$N = \text{number}$

$$= (\underbrace{a_{n-1} a_{n-2} \dots a_2 a_1 a_0}_{\text{Integer}} \cdot \underbrace{a_{-1} a_{-2} a_{-3} \dots a_{-m}}_{\text{Fraction}})_r$$

radix point

$a_j = \text{digits}$

$r = \text{radix}$

$0 \leq a_j < r$, always holds.

- Examples: (radix = base)

$$\begin{aligned} (353.12)_{r=10} &= 3 \times 10^2 + \\ &5 \times 10^1 + \\ &3 \times 10^0 + \\ &1 \times 10^{-1} + \\ &2 \times 10^{-2} \end{aligned}$$

$$\begin{aligned} (1010.01)_{r=2} &= 1 \times 2^3 + \\ &0 \times 2^2 + \\ &1 \times 2^1 + \\ &0 \times 2^0 + \\ &0 \times 2^{-1} + \\ &1 \times 2^{-2} \end{aligned}$$

General Polynomial:

$N = \text{number}$

$$= \sum_{i=-m}^{n-1} a_i r^i$$

$$N = N_I + N_F$$

$$\begin{aligned} &= a_{n-1} r^{n-1} + a_{n-2} r^{n-2} + a_{n-3} r^{n-3} + \dots + a_2 r^2 + a_1 r^1 + a_0 r^0 + \\ &\quad a_{-1} r^{-1} + a_{-2} r^{-2} + a_{-3} r^{-3} + \dots + a_{-m} r^{-m} \end{aligned}$$

• Non-numeric

o Characters

- ASCII: 1 B for each of $2^8 = 256$ English, control and special characters (Latin-1)

F	E	E	>	<	f	j	÷	≈	°	-	√	⊗	2	□	□
E	ρ	σ	τ	υ	φ	χ	ψ	ω	ш	щ	ъ	ы	э	ю	я
D	μ	π	υ	φ	χ	ψ	ω	ш	щ	ъ	ы	э	ю	я	
C	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂
B	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂
A	а	б	в	г	д	е	ж	з	и	к	л	м	н	о	п
9	р	с	т	у	ф	х	ц	ч	ш	щ	ъ	ы	э	ю	я
8	а	б	в	г	д	е	ж	з	и	к	л	м	н	о	п
7	р	с	т	у	ф	х	ц	ч	ш	щ	ъ	ы	э	ю	я
6	'	a	b	c	d	e	f	g	h	i	j	k	l	m	n
5	P	Q	R	S	T	U	V	W	X	Y	Z	[\]	^
4	@	A	B	C	D	E	F	G	H	I	J	K	L	M	N
3	0	1	2	3	4	5	6	7	8	9	:	<	=	>	?
2	!	"	#	\$	%	&	'	()	*	+	,	-	.	/
1	␣	␣	␣	␣	␣	␣	␣	␣	␣	␣	␣	␣	␣	␣	␣
0	␣	␣	␣	␣	␣	␣	␣	␣	␣	␣	␣	␣	␣	␣	␣
H	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E

From: <http://www.asciitable.com/>

character 1 byte

ASCII: "A" = $0100\ 0001 = 41$

"B" = $0100\ 0010 = 42$

"C" = $0100\ 0011 = 43$

⋮

"ECE 2500" = $45\ 43\ 45\ 20\ 32\ 35\ 30\ 30$

E C E sp 2 5 0 0

= 8 bytes


- UNICODE: $2^{24} \sim 17$ million characters with code points spread over 2 or 3B (UTF-16 or 24).
Handles international characters & emoticons

Code	Browser	Appl	Goog	Twtr	One	FB	Sams.	Wind.
U+1F914								

From: <https://unicode.org/emoji/charts/full-emoji-list.html>


- Color Codes

From: howstuffworks.com/lcd5.htm

 

- More html examples:
immigration-usa.com/html_colors.html
- 24 bit color $\rightarrow 2^{24} \sim 17$ million colors
 - Red 1 B \Rightarrow 256 shades
 - Green 1 B \Rightarrow 256 shades
 - Blue 1 B \Rightarrow 256 shades

Binary arithmetic:

 

- Bit by bit addition is done right to left, with **carry bits**

- Examples: Adding

$$\begin{array}{r}
 3 \quad 00011 \\
 +4 \quad +00100 \\
 \hline
 7 \quad 00111
 \end{array}
 \quad
 \begin{array}{r}
 5 \quad 00101 \\
 +5 \quad +00101 \\
 \hline
 10 \quad 01010
 \end{array}
 \quad
 \begin{array}{r}
 5 \quad 00101 \\
 +7 \quad +00111 \\
 \hline
 12 \quad 01100
 \end{array}$$

- Subtraction can be done by employing **borrow bits**, or more simply, by adding something called a 2's complement.

- Examples:

$$\begin{array}{r}
 10 \quad 01010 \\
 -6 \quad -00110 \\
 \hline
 4 \quad 00100
 \end{array}
 \quad
 \begin{array}{r}
 10 \quad 01010 \\
 +(-6) \quad +11010 \text{ (2's C)} \\
 \hline
 4 \quad 100100 \\
 \text{↑ overflow}
 \end{array}$$

- The concept of a *complement* of a decimal number:

$-N$ 10's C

$-1 \rightarrow 9$	$10 \rightarrow 10$
$-2 \rightarrow 8$	$-6 \rightarrow +4$
$-3 \rightarrow 7$	$4 \rightarrow 14$
$-4 \rightarrow 6$	$8 \rightarrow 8$
$-5 \rightarrow 5$	$-6 \rightarrow +4$
$-6 \rightarrow 4$	$2 \rightarrow 12$
$-7 \rightarrow 3$	$7 \rightarrow 7$
$-8 \rightarrow 2$	$-9 \rightarrow +1$
$-9 \rightarrow 1$	$-2 \rightarrow 8 \rightarrow -2$

- 2's complement procedure:

- Reverse all the bits of N
- Add 1 to the result. This is N^* .
- The sign of N^* (as well as N) is shown by the most significant bit: 0 = "+"; 1 = "-"
- Examples:

$$\begin{array}{r}
 \text{sign bit} = 1 \rightarrow \\
 N = 6 = 00110 \\
 \hline
 11001 \quad \text{step \#1} \\
 +1 \quad \text{step \#2} \\
 \hline
 -N = N^* = -6 = 11001 \\
 \text{sign bit} = 1 \rightarrow
 \end{array}$$

$$\text{eg } N^* = 11110 \text{ what is } -N?$$

$$\begin{array}{r}
 00001 \quad \text{step \#1} \\
 +1 \quad \text{step \#2} \\
 \hline
 00010 = N \therefore -N = -2
 \end{array}$$

- All the 2's complement numbers that fit into a byte.
 - 127 positive numbers N (sign bit = 0)
 - 128 negative numbers N^* (sign bit = 1)

- Zero (not shown)

N	decimal	$N^* = -N$	decimal
00000001	= 1	11111111	= -1
00000010	= 2	11111110	= -2
00000011	= 3	11111101	= -3
00000100	= 4	11111100	= -4
00000101	= 5	11111011	= -5
00000110	= 6	11111010	= -6
⋮	⋮	⋮	⋮
01111110	= 126	10000010	= -126
01111111	= 127	10000001	= -127
x	= 128	10000000	= -128


Error Correction Codes (ECC):

- Provides self-correction of errors that occur in the data when transporting data
 - Scratched disk alter recorded data:




From: hardwaresecrets.com/

 - Cosmic rays flip one bit in a 4GB chip everyday:




From: spectrum.ieee.org/

- Defaced QR code:

 

From: hwww.i-programmer.info


- Reed-Solomon ECC code in QR:

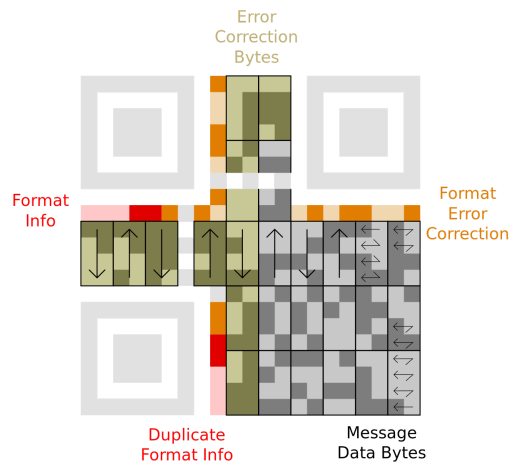

en.wikiversity.org/wiki/Reed%E2%80%93Solomon_codes_for_coders

Quiz #1 & selected solutions

BOOLEAN ALGEBRA

 

(Photo credit: Vic Lee, King Features Syndicate)

Some Preliminaries...

Binary numbers can also be used to represent truth or **logic values**.

Logic defined: the process of classifying information.

Binary logic (or more commonly, *digital logic*) is the process of classifying information into two distinct classes, e.g.

(TRUE, FALSE) = truth values

(Yes, No)

(CLOSE, OPEN) = relay positions

blown, intact = fuse state

(ON, OFF) = switch positions

(1, 0) = **binary numbers**, or (**Logic 1**, **Logic 0**)

Logic design is based upon the **three logic operators**

Binary Logic Operations (Variables)

- **AND:** $z = x \cdot y$
- **OR:** $z = x + y$
- **NOT:** $z = x'$


Binary Logic Operations

OR	XOR	AND
$0 + 0 = 0$	$0 \oplus 0 = 0$	$0 \cdot 0 = 0$
$0 + 1 = 1$	$0 \oplus 1 = 1$	$0 \cdot 1 = 0$
$1 + 0 = 1$	$1 \oplus 0 = 1$	$1 \cdot 0 = 0$
$1 + 1 = 1$	$1 \oplus 1 = 0$	$1 \cdot 1 = 1$

Two Level Logic Circuits with AND/OR/XOR gates:


From: computer.howstuffworks.com/boolean1.htm

 - **AND-OR circuits** (sum of product = *SOP*)



- **OR-AND circuits** (product of sum = *POS*)

2. **OR-AND:**

 

These circuits can also be described algebraically with the use of an algebra system for logic variables called...

Boolean Algebra

- **Fundamental properties of Boolean Algebra:** Each x, y and z are elements of $B = \{0, 1\}$

1. **Identities:** (P3, P4) (Dual)

$x + 0 = x$	$x \cdot 1 = x$
$x + 1 = 1$	$x \cdot 0 = 0$

Also Idempotency: (P6)

$x + x = x$	$x \cdot x = x$
-------------	-----------------

2. **Commutativity:** (P1)

$$x+y = y+x \quad x \cdot y = y \cdot x$$

3. **Associativity:** (P2)

$$x+(y+z) = (x+y)+z \quad x \cdot (y \cdot z) = (x \cdot y) \cdot z$$

4. **Distributivity:** (P8)

$$x+(y \cdot z) = (x+y) \cdot (x+z) \quad x \cdot (y+z) = x \cdot y + x \cdot z$$

5. **Existence of the complement:** (P5)

There exists an element x' , called NOT x , such that

$$x+x' = 1 \quad x \cdot x' = 0$$

6. **Involution:** (P7)

$$(x')' = x$$

7. **Absorption:** (P12)

$$x+xy = x \quad x(x+y) = x$$

8. **Adjacency:** (P9)

$$xy+xy' = x \quad (x+y) \cdot (x+y') = x$$

9. **DeMorgan's Law:** (P11)

$$(x+y+z)' = x'y'z' \quad (x \cdot y \cdot z)' = x'+y'+z'$$

• **Duality:** Left and right hand properties above are *duals*

- A dual may be derived by interchanging

- 1 and 0
- \cdot (AND) and $+$ (OR)

- *Examples:*


$$\begin{array}{ll} x+0 = x & x \cdot (x+y) = x \\ \downarrow \downarrow & \downarrow \downarrow \\ x \cdot 1 = x & x + xy = x \end{array}$$

Boolean Functions and Logic Circuits

- Boolean function f
 - $f(A, B, C)$ is an algebraic expression of A, B, C
 - A, B, C are Boolean variables
- Boolean functions are implemented by logic circuits
- Boolean functions may be simplified, resulting in simpler logic circuits
- Circuits and functions may be verified by constructing a truth table
- *Example #1:*
 - Derive a logic circuit from a Boolean function:


$$f(A, B, C) = \underbrace{A \cdot B}_{\text{products}} + \underbrace{A \cdot B \cdot \bar{C}}_{\text{Sum}} = \text{SOP} \\ = \text{sum of products}$$

Circuit (1)

 


 - *Example #2:*

- Derive a Boolean function for a half adder:



 - Make a full adder from two half adders:



Example#3

- Simplify the Boolean function of Example#1 by pattern matching terms with the Boolean properties above:

Boolean Algebra
(pattern matching)

$$f = AB + \underbrace{ABC}_{\text{pattern}} \checkmark$$

Let $\begin{cases} x = AB \\ y = C \end{cases}$

$$\underbrace{x + xy}_{\text{pattern}} = x$$

$$\therefore f = \underline{\underline{AB}}$$

$\boxed{A \cdot B = f}$ Circuit ②

- Compare before and after circuits with a truth table:

Truth Table:

ABC	② $A \cdot B$	minterm ABC	① $f = AB + ABC$
000	0	0	$0 + 0 = 0$
001	0	0	$0 + 0 = 0$
010	0	0	$0 + 0 = 0$
011	0	0	$0 + 0 = 0$
100	0	0	$0 + 0 = 0$
101	0	0	$0 + 0 = 0$
110	1	1	$1 + 1 = 1$
111	1	0	$1 + 0 = 1$

← Same →

- Example #4: More simplifications

$$f = A\bar{B}\bar{C} + \bar{B}$$

$$\underbrace{A\bar{B}\bar{C}}_y + \bar{B} \quad \underbrace{xy + x = x}_{\text{pattern}}$$

$$\text{Let } \begin{cases} x = \bar{B} \\ y = A\bar{C} \end{cases}$$

$$\therefore f = x = \bar{B} \checkmark$$

$$f = ABC + A\bar{B}C$$

$$\underbrace{ABC}_x + \underbrace{A\bar{B}C}_x \quad \underbrace{xy + x\bar{y} = x}_{\text{pattern}}$$

$$\text{Let } \begin{cases} x = AC \\ y = \bar{B} \end{cases}$$

$$\therefore f = x = AC \checkmark$$

- Example #5: DeMorgan's Law

$$F = \bar{A}\bar{B} + C + D$$

$$\bar{F} = ? \quad \underbrace{\bar{A}\bar{B}}_x + \underbrace{C}_y + \underbrace{D}_z$$

pattern:

$$\overline{x+y+z} = \bar{x} \cdot \bar{y} \cdot \bar{z}$$

$$\begin{aligned} \bar{F} &= \bar{\bar{A}\bar{B}} \cdot \bar{C} \cdot \bar{D} \\ &\quad \underbrace{x \cdot y \rightarrow \text{pattern: } \bar{x} + \bar{y}}_{\text{DeM}} \\ &= (\bar{A} + \bar{B}) \cdot \bar{C} \cdot \bar{D} \\ &= (A + B) \bar{C} \cdot \bar{D} \end{aligned}$$

Quiz #2 & selected solutions

LOGIC GATES AND CIRCUITS

DeMorgan's Laws Shows Equivalent Graphical Symbols for Logic Gates: Examples are given to describe

- NAND gate drawn with an OR symbol

$$\begin{aligned} x \text{ AND } y &= \overline{\overline{x \text{ AND } y}} \quad \text{DeM} \\ &= \overline{x + y} \quad \text{ORing} \end{aligned}$$

- NOR gate drawn with an AND symbol

$$\begin{aligned} x \text{ NOR } y &= \overline{x + y} \quad \text{DeM} \\ &= \overline{\overline{\overline{x + y}}} \quad \text{ANDing} \\ &= \overline{x \cdot y} \end{aligned}$$

- NOTs built from NANDs, NORs and XORs


$$x \text{ NAND } x = \overline{x \cdot x} = \bar{x} \quad x \text{ NOR } x = \overline{x + x} = \bar{x}$$

$$x \text{ AND } 1 = \overline{x \cdot 1} = \bar{x} \quad x \text{ OR } 0 = \overline{x + 0} = \bar{x}$$


$$\text{XOR: } x \text{ XOR } x = \bar{x}$$

Two Level Logic Circuits with Other Gates: Examples are given to describe

 
- **NAND-NAND** circuits = **AND-OR** circuits; makes **SOP** functions
(Leading NAND looks like an OR)



 
- **NOR-NOR** circuits = **OR-AND** circuits; makes **POS** functions
(Leading NOR looks like an AND)



- **Example: NAND-NOR Combination**

 

 
- **Example: Carry-lookahead adder logic**
 - Most heavily designed circuit in the history of electronics
 - NOT, NAND, NOR, XOR combination
 - Gate fronts and backs match so bubbles cancel



CMOS Implementation of Logic Gates

 Examples are shown to implement **NAND**, **NOR**, and **NOT** gates from elementary **NMOS** and **PMOS** transistors.


- **CMOS** transistors = NMOS plus PMOS
- Current flows between the Source and the Drain
- The Gate voltage controls the conduction value between the Source and Drain:




The NMOS transistor may be configured to operate in one of three different states, as determined by the **voltage** at the gate terminal V_G :

- Three states of a **NMOS** and **PMOS** transistors:


- **OFF state (Nonconducting)**

 

- **ON state (Conducting)**

 


- **Resistive state (A resistor)**

 


- **NAND**, **NOR** and **NOT** gates can be constructed from two to four transistors.


- **NOT**

 

- **NAND**

 


- **NOR**

 

- **AND** and **OR** gates
 - Require at least six **CMOS** transistors.

- Example: OR gate = NOR plus NOT

 

- Integrated circuit layout for **NOT**, **NAND** and **NOR** gates, using CMOS.
- Zoom down inside an IC to see gates!

Quantum Computing Implementation of Logic Gates


- **Pauli X (NOT) gate**

$|0\rangle$ State becomes $|1\rangle$ State




- **CNOT gate** (using Toffoli)

$|0\rangle$ State becomes $|1\rangle$ State if the Control is $|1\rangle$

 

- **AND gate** (using CCNOT Toffoli)

$0 \oplus xy = xy$

 


- **H gate**

$|0\rangle$ State becomes 50% superimposed with $|1\rangle$ State



- Example Quantum Full Adder Circuit

 

(Image: thequantuminsider.com)

Quiz #3 & selected solutions

MINTERMS

Suppose we want to expand a certain **SOP** function f_I into canonical form whereby each resulting product term contains a literal of every independent variable of f_I .

$$\begin{aligned}
 f_I(A, B, C) &= \bar{A} \cdot B + B \cdot \bar{C} + A \cdot B \cdot C = \text{SOP} \\
 &= \bar{A}B(C + \bar{C}) + B\bar{C}(A + \bar{A}) + ABC \\
 f_I(A, B, C) &= \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC = \text{canonical SOP}
 \end{aligned}$$

↖ minterms ↗

The product terms above are called **minterms**, the properties of which are now be presented.

Minterm Properties and Notation

- A **minterm** is a product term which produces a single **1** in a truth table

row	ABC	$\bar{A}\bar{B}\bar{C}$ m_0	$\bar{A}B\bar{C}$ m_1	$A\bar{B}\bar{C}$ m_2	ABC m_3	f_I	\bar{f}_I
0	000	0	0	0	0	0	1
1	001	0	0	0	0	0	1
2	010	0	0	0	0	0	1
3	011	0	0	0	0	0	1
4	100	0	0	0	0	0	1
5	101	0	0	0	0	0	1
6	110	0	0	0	0	0	1
7	111	0	0	0	0	0	1

- The minterm which yields a **1** in row i is denoted as minterm m_i
- Express f in terms of minterms:
 - Compose a minterm list for f . (An atomic list)

◦ Example:

$$\begin{aligned} f_1 &= \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \\ &= m_2 + m_3 + m_6 + m_7 \\ &= \sum m(2, 3, 6, 7) \end{aligned}$$

• Additional properties of minterm lists

- $f = \sum m(\text{row\#s where } f = 1)$
- $f' = \sum m(\text{row\#s where } f = 0)$
- $\sum m(\text{all row\#s}) = 1$

• Minterm index i

- Obtained by determining the row code for which $m_i = 1$
- Example:

$$\begin{aligned} \bar{A}\bar{B}\bar{C} &= 1 \text{ where?} \\ \downarrow \downarrow \downarrow \\ \textcircled{0} \textcircled{1} \textcircled{0} &\text{ in row 2} \\ &\quad \quad \quad \downarrow \\ &\quad \quad \quad 2 \\ \therefore \bar{A}\bar{B}\bar{C} &= m_2 \end{aligned}$$

Quiz #4 & selected solutions (also includes *Maxterms* discussed below)


K-MAPS

Karnaugh Maps

What is a K-map? It is a graphical tool that quickly finds minimal algebraic forms of Boolean functions. The *SOP* forms are discussed here; *POS* forms are described in a later section.


Karnaugh Map Properties

 - Each cell in a K-map for a function f corresponds to a row of the truth table describing f
- Cell i is a place mark for minterm m_i .
- K-map labels identify the *coincidence of literals* to combine adjacent minterm.




Sizes of K-maps


- Example: 2 variable

 

- Example: 3 variable

 


- Example: 4 variable

 

Procedure for Plotting SOP Functions on a K-map

 - Determine the minterms m_i contained in f (found by observing the rows where $f = 1$ in the truth table).
- Plot the 1's of the function to be minimized on the K-map.
 - For each minterm m_i in f , enter a 1 in cell i .
 - Example:




- For each don't care contained in f , enter a d (or x) in the associated K-map cell (see example later).

Procedure for reading minimal SOP expressions from K-maps


- Draw loops around adjacent 1-entries (cells with 1's) in largest groups possible.
 - Group size in a power of two (e.g. 1 cell, 2 cells, 4 cells, 8 cells, etc.)

- Example:

 


- Cells over the left and right edges, or the upper and lower edges are also *defined* to be adjacent.

- Example:

 

- 1-entries not adjacent to other 1-entries are circled as groups of one.


- Example:

 

- Discard **redundant groupings**


- Discard those entries covered entirely by other groups

- Example:

 

- For each group (as seen in the several examples above),
 - **Read off the coincident literals**, by exploiting K-map labels
 - **AND** those literals together to form products formed by the groups
 - **OR** the resulting products to create a SOP expression


- Examples:

 

Map Simplification Resulting from Don't Cares

- Don't care = d (or X) = $\{0,1\}$ (either a 0 or a 1)
- Group 1-entries as before, but

 - Also include any **d**-entries which serve to increase the size of the group of **1**'s
- Treat unused **d**-entries as **0**-entries
- Must have at least one **1**-entry in all groups
- *Example:*



- Never group cells consisting **entirely** of don't care entries. This results in a redundant group.

Quiz #5 & selected solutions (includes POS usages)

MAXTERMS & K-MAPS

Maxterm Properties and Notation

Now we want to consider expanding a certain **POS** function f_2 into canonical form whereby each resulting sum term contains a literal of every independent variable of f_2 .

$$\begin{aligned}
 f_2(A, B, C) &= (A+B) \cdot (\bar{A}+B+C) \cdot (\bar{A}+B+\bar{C}) = \text{POS} \\
 &= (A+B+C) \cdot (A+B+\bar{C}) \cdot (\bar{A}+B+C) \cdot (\bar{A}+B+\bar{C}) = \text{canonical POS}
 \end{aligned}$$

sum product
maxterms

The sum terms above are called **Maxterms**, the properties of which now follow.

- A **Maxterm** is a sum term which produces a single **0** in a truth table

$n=3$		M_0	M_1	M_4	M_5	f_2	\bar{f}_2
row	ABC	$(A+B+C)$	$(A+B+\bar{C})$	$(\bar{A}+B+C)$	$(\bar{A}+B+\bar{C})$		
0	000	0	1	1	1	0	1
1	001	1	0	1	1	0	1
2	010	1	1	1	1	1	0
3	011	1	1	1	1	1	0
4	100	1	1	0	1	0	1
5	101	1	1	1	0	0	1
6	110	1	1	1	1	1	0
7	111	1	1	1	1	1	0

- Maxterm which yields a **0** in row i is denoted as maxterm M_i
- Expressing f in terms of Maxterms:
 - Compose a Maxterm list for f . (An atomic list)

- Example:

$$\begin{aligned}
 f_2 &= (A+B+C) \cdot (A+B+\bar{C}) \cdot (\bar{A}+B+C) \cdot (\bar{A}+B+\bar{C}) \\
 &= M_0 \cdot M_1 \cdot M_4 \cdot M_5 \\
 &= \prod M(0,1,4,5)
 \end{aligned}$$

- Additional properties of Maxterm lists
 - $f = \prod M(\text{row\#s where } f = 0)$
 - $f' = \prod M(\text{row\#s where } f = 1)$
 - $\prod M(\text{all row\#s}) = 0$
- Maxterm index i
 - Obtained by determining the row code for which $M_i = 1$
 - Example:

$$\begin{aligned}
 \bar{A}+B+\bar{C} &= 0 \text{ where?} \\
 \downarrow \downarrow \downarrow & \\
 \begin{array}{|c|c|c|} \hline 1 & 0 & 1 \\ \hline \end{array} & \text{ in row } \underline{5} \\
 \downarrow & \\
 \therefore \bar{A}+B+\bar{C} &= M_5
 \end{aligned}$$

Other Properties of minterms and Maxterms

- $f = \sum m(\text{row\#s}) = \prod M(\text{opposite row\#s})$
 $f = \prod M(\text{row\#s}) = \sum m(\text{opposite row\#s})$
- If $f = \sum m(\text{row\#s})$ then $f' = \sum m(\text{opposite row\#s})$
 If $f = \prod M(\text{row\#s})$ then $f' = \prod M(\text{opposite row\#s})$
 - Examples:

for our 2 tables earlier:

$$f_1 = \sum m(2,3,6,7) = \prod M(0,1,4,5) = f_2$$

$$\bar{f}_1 = \sum m(0,1,4,5) = \prod M(2,3,6,7) = \bar{f}_2$$

- $m_i' = M_i$
 $M_i' = m_i$
 - Examples:

$$m_i + M_i = m_i + \bar{m}_i = 1$$

($x + \bar{x} = 1$)


$$m_i \cdot \bar{M}_i = m_i \cdot m_i = m_i$$

($x \cdot x = x$)

K-Map POS Properties


- Cell i is a place mark for Maxterm M_i .

 - K-map labels identify the *coincidence of literals* to combine adjacent Maxterms.



Procedure for plotting and reading minimal POS expressions from K-maps

 - Plot the 0's of the function** to be minimized on a K-map.
 - For each maxterm M_i in f , enter a **0** in cell i .
 - Example:



- Draw **loops** around **adjacent 0-entries**.
- For each group
 - Read off the complement** of the **coincident literals** covering the group
 - OR** those literals together to form sums
 - AND** the resulting sums to create a product
 - Example:

